

**AB01**  
**Silicon, Zener, LED**  
**Diode Characteristics**

**Operating Manual**  
**Ver.1.1**

An ISO 9001 : 2000 company



94-101, Electronic Complex Pardesipura,  
Indore- 452010, India

Tel : 91-731- 2570301/02, 4211100

Fax: 91- 731- 2555643

e mail : [info@scientech.bz](mailto:info@scientech.bz)

Website : [www.scientech.bz](http://www.scientech.bz)

Toll free : 1800-103-5050



# CERTIFICATE

The Certification Body for  
Quality Management Systems  
of TÜV Rheinland India Pvt. Ltd.

certifies in accordance with  
TÜV Rheinland Group procedures that

## Sciencetech Technologies Pvt. Ltd.

Unit-1: 94-101, Electronics Complex, Pardeshi Pura,  
Indore – 452 010, Madhya Pradesh, India

Unit-2: 90-91, Electronics Complex, Pardeshi Pura,  
Indore – 452 010, Madhya Pradesh, India

has established and applies a quality management system for

**Design, Manufacture of Electronic Test & Measuring  
Instruments, Training Products for Electrical & Electronics  
Education and Providing Technology Training**

An audit was performed, Report No. 07930  
Proof has been furnished that the requirements according to

**DIN EN ISO 9001: 2000**

are fulfilled.

The certificate is valid until 2010-11-20  
Certificate Registration No. **85 100 001 07930**



Bangalore, 2007-11-21

The validity of this certificate is subject to timely completion of Surveillance audits as agreed  
in the Contract. The Validity of the Certificate can be verified under [www.tuv.com](http://www.tuv.com) with the Identification No. 9105027653

The certification Body of  
TÜV Rheinland India Pvt. Ltd.

04/11/NABCB/00

[www.tuv.com](http://www.tuv.com)

**AB01**  
**Silicon, Zener, LED**  
**Diode Characteristics**

**Table of Contents**

1.	Introduction	4
2.	Theory	6
3.	Experiments	8
	• Experiment 1	10
	Study of V-I characteristics of Silicon diode	
	• Experiment 2	13
	Study of V-I characteristics of Zener diode	
	• Experiment 3	16
	Study of V-I characteristics of Light Emitting Diode (LED)	
4.	Warranty	19
5.	List of Accessories	19

**RoHS Compliance**



Scientech Products are RoHS Complied.

RoHS Directive concerns with the restrictive use of Hazardous substances (Pb, Cd, Cr, Hg, Br compounds) in electric and electronic equipments.

Scientech products are “Lead Free” and “Environment Friendly”.

It is mandatory that service engineers use lead free solder wire and use the soldering irons upto (25 W) that reach a temperature of 450°C at the tip as the melting temperature of the unleaded solder is higher than the leaded solder.

### Introduction

**AB01** is a compact, ready to use **Diode Characteristics** experiment board. This is useful for students to plot V-I characteristics of Si Diode, Zener Diode, and light Emitting Diode in forward as well as in reverse bias region of operation. It can be used as stand alone unit with external DC power supply or can be used with **Scientech Analog Lab ST2612** which has built in DC power supply, AC power supply, function generator, modulation generator, continuity tester, toggle switches, and potentiometer.

#### List of Boards :

<b>Model</b>	<b>Name</b>
<b>AB02</b>	Transistor characteristics (CB NPN)
<b>AB03</b>	Transistor characteristics (CB PNP)
<b>AB04</b>	Transistor characteristics (CE NPN)
<b>AB05</b>	Transistor characteristics (CE PNP)
<b>AB06</b>	Transistor characteristics (CC NPN)
<b>AB07</b>	Transistor characteristics (CC PNP)
<b>AB08</b>	FET characteristics
<b>AB09</b>	Rectifier Circuits
<b>AB10</b>	Wheatstone bridge
<b>AB11</b>	Maxwell's Bridge
<b>AB12</b>	De Sauty's Bridge
<b>AB13</b>	Schering Bridge
<b>AB14</b>	Darlington Pair
<b>AB15</b>	Common Emitter Amplifier
<b>AB16</b>	Common Collector Amplifier
<b>AB17</b>	Common Base Amplifier
<b>AB18</b>	RC-Coupled Amplifier
<b>AB19</b>	Cascode Amplifier
<b>AB20</b>	Direct Coupled Amplifier
<b>AB21</b>	Class A Amplifier
<b>AB22</b>	Class B Amplifier (Push Pull Emitter Follower)
<b>AB23</b>	Class C Tuned Amplifier
<b>AB24</b>	Transformer Coupled Amplifier
<b>AB25</b>	Phase Locked Loop (FM Demodulator & Frequency Divider / Multiplier)
<b>AB26</b>	FET Amplifier
<b>AB27</b>	Voltage Controlled Oscillator
<b>AB28</b>	Multivibrator (Monostable / Astable)
<b>AB29</b>	F-V and V-F Converter
<b>AB30</b>	V-I and I-V Converter
<b>AB31</b>	Zener Voltage Regulator
<b>AB32</b>	Transistor Series Voltage Regulator
<b>AB33</b>	Transistor Shunt Voltage Regulator
<b>AB35</b>	DC Ammeter
<b>AB37</b>	DC Ammeter (0-2mA)

---

**AB01**

---


<b>AB39</b>	Instrumentation Amplifier
<b>AB41</b>	Differential Amplifier (Transistorized)
<b>AB42</b>	Operational Amplifier (Inverting /Non-inverting / Differentiator)
<b>AB43</b>	Operational Amplifier (Adder/Scalar)
<b>AB44</b>	Operational Amplifier (Integrator/ Differentiator)
<b>AB45</b>	Schmitt Trigger and Comparator
<b>AB49</b>	K Derived Filter
<b>AB51</b>	Active filters (Low Pass and High Pass)
<b>AB52</b>	Active Band Pass Filter
<b>AB54</b>	Tschebyscheff Filter
<b>AB56</b>	Fiber Optic Analog Link
<b>AB57</b>	Owen's Bridge
<b>AB58</b>	Anderson's Bridge
<b>AB59</b>	Maxwell's Inductance Bridge
<b>AB64</b>	RC – Coupled Amplifier with Feedback
<b>AB66</b>	Wien Bridge Oscillators
<b>AB67</b>	Colpitt Oscillator
<b>AB68</b>	Hartley Oscillator
<b>AB80</b>	RLC Series and RLC Parallel Resonance
<b>AB82</b>	Thevenin's and Maximum Power Transfer Theorem
<b>AB83</b>	Reciprocity and Superposition Theorem
<b>AB84</b>	Tellegen's Theorem
<b>AB85</b>	Norton's theorem
<b>AB88</b>	Diode Clipper
<b>AB89</b>	Diode Clampers
<b>AB90</b>	Two port network parameter
<b>AB91</b>	Optical Transducer (Photovoltaic cell)
<b>AB92</b>	Optical Transducer (Photoconductive cell/LDR)
<b>AB93</b>	Optical Transducer (Phototransistor)
<b>AB96</b>	Temperature Transducer (RTD & IC335)
<b>AB97</b>	Temperature Transducer (Thermocouple)
<b>AB101</b>	DSB Modulator and Demodulator
<b>AB102</b>	SSB Modulator and Demodulator
<b>AB106</b>	FM Modulator and Demodulator

and many more.....

## Theory


### Introduction :

A *diode* is an electrical device allowing current to move through it in one direction with far greater ease than in the other. The most common type of diode in modern circuit design is the *semiconductor* diode, although other diode technologies exist. Semiconductor diodes are symbolized in schematic diagrams as shown below

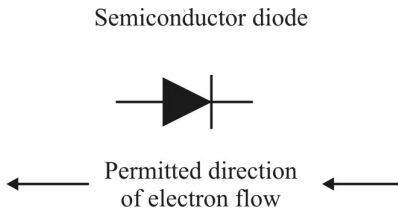

**Figure 1**

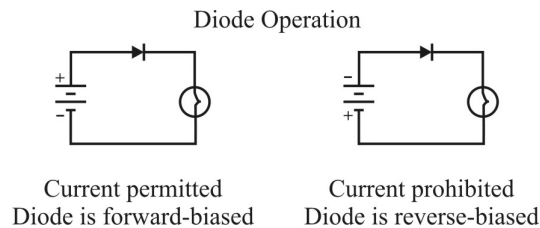When placed in a simple battery-lamp circuit, the diode will either allow or prevent current through the lamp, depending on the polarity of the applied voltage:

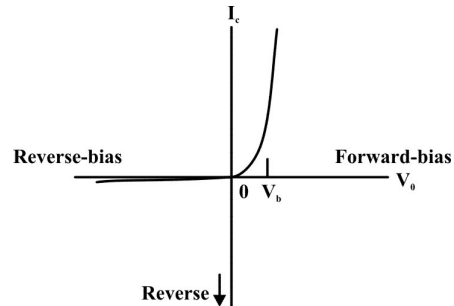


**Figure 2**

When the polarity of the battery is such that electrons are made to flow through the diode, the diode is said to be *forward-biased*. Conversely, when the battery is "backward" and the diode blocks current, the diode is said to be *reverse biased*. A diode may be thought of as a kind of switch: "closed" when forward-biased and "open" when reverse-biased.

**V-I Characteristic :**

The static voltage-current characteristics for a P-N Junction diode are shown in figure 3.

**Figure 3****Forward Characteristic :**

When the diode is in forward-biased and the applied voltage is increased from zero, hardly any current flows through the device in the beginning. It is so because the external voltage is being opposed by the internal barrier voltage  $V_B$  whose value is 0.7V for Si and 0.3V for Ge. As soon as  $V_B$  is neutralized, current through the diode increases rapidly with increasing applied supply voltage. It is found that as a little voltage of 1.0V produces a forward current of about 50mA.

**Reverse Characteristic :**

When the diode is reverse-biased, majority carrier are blocked and only a small current (due to minority carrier) flows through the diode. As the reverse voltage is increased from zero, the reverse current very quickly reaches its maximum or saturation value  $I_o$  which is also known as leakage current. It is of the order of nanoAmperes (nA) and microAmperes ( $\mu$ A) for Ge.

As seen from figure 3, when reverse voltage exceeds a certain value called breakdown voltage  $V_{BR}$ , the leakage current suddenly and sharply increases, the curve indicating zero resistance at this point.

**Zener Diode :**

It is the reverse-biased heavily-doped silicon (or germanium) P-N Junction diode which is operated in the breakdown region where current is limited by both external resistance and power dissipation of the diode. Silicon is preferred to diode because of its higher temperature and current capability. Zener breakdown occurs due to breaking of covalent bonds by the strong electric field set up in the depletion region by the reverse voltage.

It produces an extremely large number of electrons and holes, which constitute the reverse saturation current (called zener current  $I_z$ ) whose value is limited only by the external resistance in the circuit.

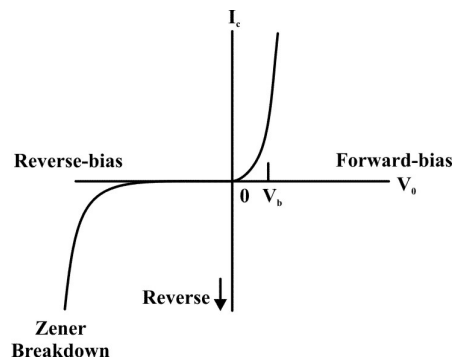
**V-I Characteristic :**

Figure 4 shows typical characteristics in the negative quadrant. The forward characteristic is simply that of an ordinary forward-biased junction diode. The important points of the reverse characteristic are  $V_z$  = Zener breakdown voltage.

$I_{z \min}$  = Minimum current to sustain breakdown

$I_{z \max}$  = Maximum Zener current limited by, maximum power dissipation. Since its reverse characteristic is not exactly vertical, the diode possesses some resistance called Zener dynamic impedance. Its value is given by  $Z_z = \Delta V_z / \Delta I_z$ .

Zener diodes are available having zener voltage of 2.4V to 200V. This voltage is temperature dependent. The product  $V_z, I_z$ , gives their power dissipation. Maximum ratings vary from 150mW to 50W.

**Figure 4**

For proper working of a Zener diode in any circuit, it is essential that it must

1. Be reverse-biased,
2. Have voltage across it greater than  $V_z$ ,
3. Be in a circuit where current is less than  $I_{z \max}$ .

**Light-emitting Diodes :**

Diodes, like all semiconductor devices, are governed by the principles described in quantum physics. One of these principles is the emission of specific-frequency radiant energy whenever electrons fall from a higher energy level to a lower energy level.

A diode intentionally designed to glow like a lamp is called a *light-emitting diode*, or *LED*. Diodes made from a combination of the elements gallium, arsenic, and phosphorus (called *gallium-arsenide-phosphide*) glow bright red, and one of some of the most common LED manufactured. By altering the chemical constituency of the PN junction, different colors may be obtained. Some of the currently available colors other than red are green, blue, and infra-red (invisible light at a frequency lower than red). Other colors may be obtained by combining two or more primary-color (red, green, and blue). The schematic symbol for an LED is a regular diode shape inside of a circle, with two small arrows pointing away (indicating emitted light)




Light emitted diode (LED)

**Figure 5**

This notation of having two small arrows pointing away from the device is common to the schematic symbols of all light-emitting semiconductor devices. Conversely, if a device is light-*activated* (meaning that incoming light stimulates it), then the symbol will have two small arrows pointing *toward* it. It is interesting to note, though, that LEDs are capable of acting as light-sensing devices: they will generate a small voltage when exposed to light, much like a solar cell on a small scale. This property can be gainfully applied in a variety of light-sensing circuits.

Because LEDs are made of different chemical substances than normal rectifying diodes, their forward voltage drops will be different. Typically, LEDs have much larger forward voltage drops than rectifying diodes, anywhere from about 1.6 Volts to over 3 Volts, depending on the color. Typical operating current for a standard-sized LED is around 20 mA. When operating an LED from a DC voltage source greater than the LED's forward voltage, a series-connected "dropping" resistor must be included to prevent full source voltage from damaging the LED. LED starts emitting light as its forward voltage reaches at a particular level and its intensity will increase further with the increase in applied forward voltage. LEDs emit no light when reverse biased. In fact, operating LEDs in reverse direction will quickly destroy them if the applied voltage is quite large. LEDs V-I characteristic curve is shown in figure 6.

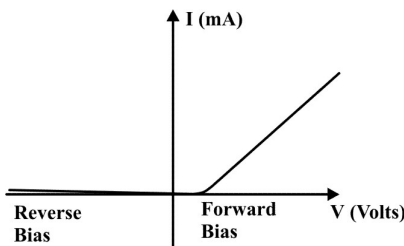**Characteristics of LED****Figure 6**

### Experiment 1

**Objective :**

**Study of characteristics of Silicon diode in :**


- 1. Forward bias**
- 2. Reverse bias**

**Equipments Needed :**

- 1. Analog board of AB01.**
- 2. DC power supplies +12V from external source or ST2612 Analog Lab.**
- 3. Digital Multimeter (2 numbers).**

**Circuit diagram :**

Circuit used to plot different characteristics of Si diode is shown in figure 7.

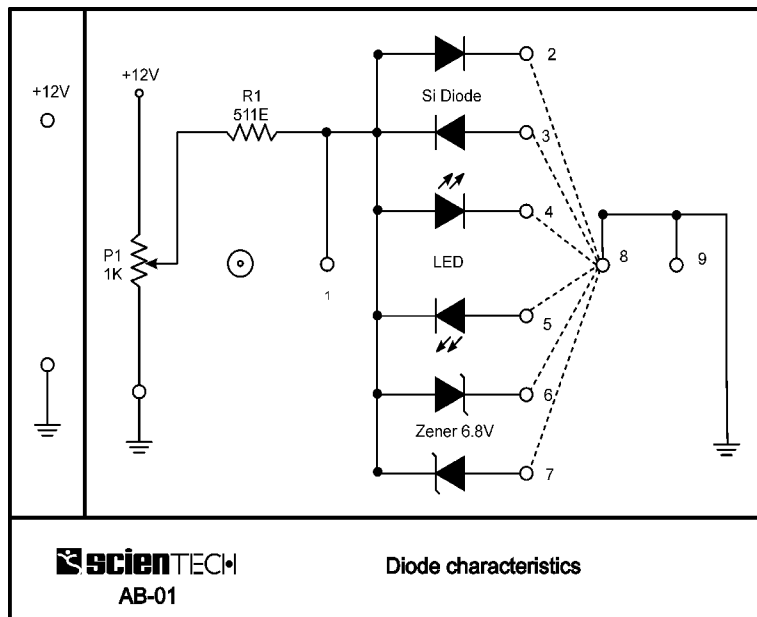

**Figure 7**

**Procedure :**

- Connect +12V DC power supplies at their indicated position from external source or **ST2612 Analog Lab**.
- To plot forward characteristics proceed as follows
  1. Rotate potentiometer  $P_1$  fully in CCW (counter clockwise direction).
  2. Connect Ammeter between test point 2 and 8 to measure diode current  $I_D$  (mA).
  3. Connect one voltmeter between test point 1 and 9 to measure voltage  $V_D$  diode
  4. Switch 'On' the power supply.
  5. Vary the potentiometer  $P_1$  so as to increase the value of diode voltage  $V_D$  from zero to 1V in step and measure the corresponding values of diode current  $I_D$  in an observation Table 1.
  6. Plot a curve between diode voltage  $V_D$  and diode current  $I_D$  as shown in figure 3 (First quadrant) using suitable scale with the help of observation Table 1. This curve is the required forward characteristics of Si diode.

**Observation Table 1 :**

S. No.	Diode Voltage (VD)	Diode current $I_D$ (mA)
1.	0.0V	
2.	0.1V	
3.	0.2V	
4.	0.3V	
5.	0.4V	
6.	0.5V	
7.	0.6V	
8.	0.7V	
9.	0.8V	
10.	0.9V	
11.	1.0V	

- To plot Reverse characteristics of a Si diode proceed as follows
  1. Rotate potentiometer  $P_1$  fully in CCW (counter clockwise direction).
  2. Connect Ammeter between test point 3 and 8 to measure diode current  $I_D$  (nA).
  3. Connect one voltmeter between test point 1 and 9 to measure voltage  $V_D$  diode
  4. Switch 'On' the power supply.
  5. Vary the potentiometer  $P_1$  so as to increase the value of diode voltage  $V_D$  from zero to 10V in step and measure the corresponding values of diode current  $I_D$  in an observation Table 2.

6. Plot a curve between diode voltage  $V_D$  and diode current  $I_D$  as shown in figure 3 (third quadrant) using suitable scale with the help of observation Table 2. This curve is the required forward characteristics of Si diode.

**Observation Table 2 :**

<b>S. No.</b>	<b>Diode Voltage (<math>V_D</math>)</b>	<b>Diode current <math>I_D</math> (nA)</b>
<b>1.</b>	0.0V	
<b>2.</b>	1.0V	
<b>3.</b>	2.0V	
<b>4.</b>	3.0V	
<b>5.</b>	4.0V	
<b>6.</b>	5.0V	
<b>7.</b>	6.0V	
<b>8.</b>	7.0V	
<b>9.</b>	8.0V	
<b>10.</b>	9.0V	
<b>11.</b>	10.0V	

### Experiment 2

**Objective :**

**Study of characteristics of Zener diode in**


1. **Forward bias**
2. **Reverse bias**

**Equipments Needed :**

1. Analog board of **AB01**
2. DC power supplies +12V from external source or **ST2612 Analog Lab**.
3. Digital Multimeter (2 numbers).

**Circuit diagram :**

Circuit used to plot different characteristics of Zener diode is shown in figure 8

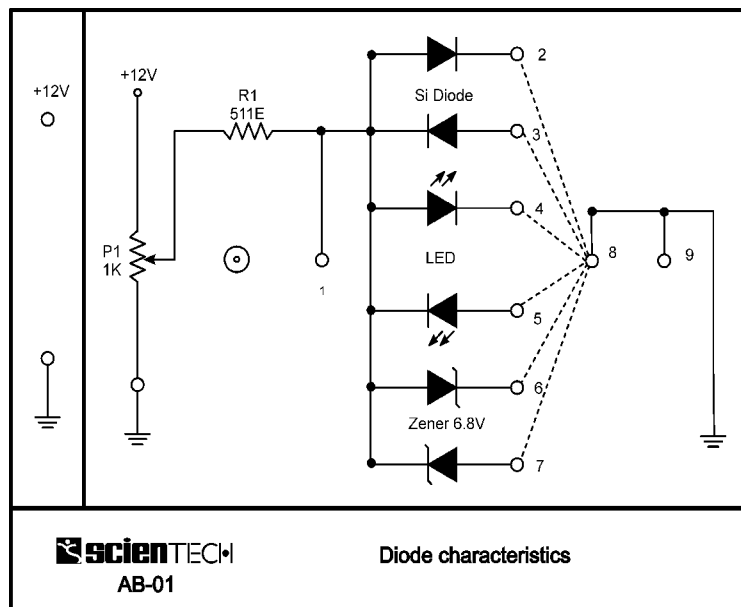

**Figure 8**

**Procedure :**

- Connect +12V DC power supplies at their indicated position from external source or **ST2612 Analog Lab**.
- To plot Forward characteristics proceed as follows:
  1. Rotate potentiometer  $P_1$  fully in CCW (counter clockwise direction).
  2. Connect Ammeter between test point 6 and 8 to measure diode current  $I_z$  (mA).
  3. Connect one voltmeter between test point 1 and 9 to measure voltage  $V_z$  diode.
  4. Switch 'On' the power supply.
  5. Vary the potentiometer  $P_1$  so as to increase the value of Zener voltage  $V_z$  from zero to 0.8 in step and measure the corresponding values of diode current  $I_z$  in an observation Table 1.
  6. Plot a curve between diode voltage  $V_z$  and diode current  $I_z$  as shown in figure 4 (First quadrant) using suitable scale with the help of observation Table 1. This curve is the required forward characteristics of zener diode.

**Observation Table 1 :**

<b>S. No.</b>	<b>Diode Voltage (<math>V_z</math>)</b>	<b>Diode current <math>I_z</math> (mA)</b>
<b>1.</b>	0.0V	
<b>2.</b>	0.1V	
<b>3.</b>	0.2V	
<b>4.</b>	0.3V	
<b>5.</b>	0.4V	
<b>6.</b>	0.5V	
<b>7.</b>	0.6V	
<b>8.</b>	0.7V	
<b>9.</b>	0.8V	

- To plot Reverse characteristics of a Zener diode proceed as follows
1. Rotate potentiometer  $P_1$  fully in CCW (counter clockwise direction).
  2. Connect Ammeter between test point 7 and 8 to measure diode current  $I_z$  (mA).
  3. Connect one voltmeter between test point 1 and 9 to measure voltage  $V_z$  diode
  4. Switch 'On' the power supply.
  5. Vary the potentiometer  $P_1$  so as to increase the value of diode voltage  $V_D$  from zero to 12V in step and measure the corresponding values of diode current  $I_z$  in an observation Table 2.
  6. Plot a curve between diode voltage  $V_z$  and diode current  $I_z$  as shown in figure 4 (third quadrant) using suitable scale with the help of observation Table 2. This curve is the required Reverse characteristics of Zener diode.

**Observation Table 2 :**

S. No.	Diode Voltage ( $V_z$ )	Diode current $I_z$ (mA)
1.		
2.		
3.		
4.		
5.		
6.		
7.		
8.		
9.		
10.		
11.		

### Experiment 3

#### Objective :

#### Study of characteristics of Light emitting diode (LED) in


1. Forward bias
2. Reverse bias

#### Equipments Needed :

1. Analog board of **AB01**
2. DC power supplies +12V from external source or **ST2612 Analog Lab**.
3. Digital Multimeter (2 numbers).

#### Circuit diagram :

Circuit used to plot different characteristics of Light Emitting Diode (LED) is shown in figure 9.

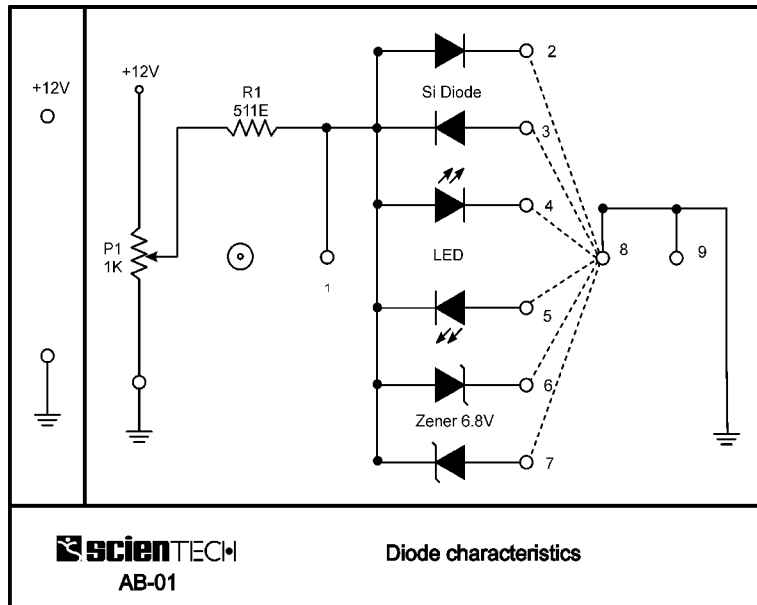

**Figure 9**

#### Procedure :

- Connect +12V DC power supplies at their indicated position from external source or **ST2612 Analog Lab**.
- To plot forward characteristics proceed as follows:
  1. Rotate potentiometer  $P_1$  fully in CCW (counter clockwise direction).
  2. Connect Ammeter between test point 4 and 8 to measure diode current  $I_D$  (mA).
  3. Connect one voltmeter between test point 1 and 9 to measure voltage  $V_D$  diode
  4. Switch 'On' the power supply.



5. Vary the potentiometer  $P_1$  so as to increase the value of diode voltage  $V_D$  from zero to maximum in steps and measure the corresponding values of diode current  $I_D$  in an observation Table 1.
6. Also consider the effect on light intensity with the change in diode voltage and diode current.
7. Plot a curve between diode voltage  $V_D$  and diode current  $I_D$  as shown in figure 5 using suitable scale with the help of observation Table 1. This curve is the required forward characteristics of Light emitting diode.

**Observation Table 1 :**

<b>S. No.</b>	<b>Diode Voltage(<math>V_D</math>)</b>	<b>Diode current <math>I_D</math> (mA)</b>
<b>1.</b>		
<b>2.</b>		
<b>3.</b>		
<b>4.</b>		
<b>5.</b>		
<b>6.</b>		
<b>7.</b>		
<b>8.</b>		
<b>9.</b>		
<b>10.</b>		

- To plot Reverse characteristics proceed as follows:
  1. Rotate potentiometer P<sub>1</sub> fully in CCW (counter clockwise direction).
  2. Connect Ammeter between test point 5 and 8 to measure diode current I<sub>D</sub>( $\mu$ A)
  3. Connect one voltmeter between test point 1 and 9 to measure voltage V<sub>D</sub> diode.
  4. Switch 'On' the power supply.
  5. Vary the potentiometer P1 so as to increase the value of diode voltage V<sub>D</sub> from zero to maximum in steps and measure the corresponding values of diode current I<sub>D</sub> in an observation Table 2.
  6. Plot a curve between diode voltage V<sub>D</sub> and diode current I<sub>D</sub> as shown in figure 5 (Third quadrant) using suitable scale with the help of observation Table 2. This curve is the required forward characteristics of Light emitting diode.

**Observation Table 2 :**

S. No.	Diode Voltage(V <sub>D</sub> )	Diode current I <sub>D</sub> (mA)
1.		
2.		
3.		
4.		
5.		
6.		
7.		
8.		
9.		
10.		
11.		

### **Warranty**

1. We guarantee the product against all manufacturing defects for 24 months from the date of sale by us or through our dealers. Consumables like dry cell etc. are not covered under warranty.
2. The guarantee will become void, if
  - a) The product is not operated as per the instruction given in the operating manual.
  - b) The agreed payment terms and other conditions of sale are not followed.
  - c) The customer resells the instrument to another party.
  - d) Any attempt is made to service and modify the instrument.
3. The non-working of the product is to be communicated to us immediately giving full details of the complaints and defects noticed specifically mentioning the type, serial number of the product and date of purchase etc.
4. The repair work will be carried out, provided the product is dispatched securely packed and insured. The transportation charges shall be borne by the customer.

For any Technical Problem Please Contact us at [service@scientech.bz](mailto:service@scientech.bz)

### **List of Accessories**

1. 2 mm Patch Cords (Red) ..... 1 No.
2. 2 mm Patch Cord (Black) ..... 1 No.
3. 2 mm Patch Cord (Blue) ..... 1 No.
4. e-Manual..... 1 No.

Updated 08-01-2009