

AB51
Active Filters
Low Pass and High Pass

Operating Manual
Ver.1.1

An ISO 9001 : 2000 company



Innovative Technology Ecosystem

94-101, Electronic Complex Pardesipura,
Indore- 452010, India

Tel : 91-731- 2570301/02, 4211100

Fax: 91- 731- 2555643

e mail : info@scientech.bz

Website : www.scientech.bz

Toll free : 1800-103-5050



CERTIFICATE

The Certification Body for
Quality Management Systems
of TÜV Rheinland India Pvt. Ltd.

certifies in accordance with
TÜV Rheinland Group procedures that

Scientech Technologies Pvt. Ltd.

Unit-1: 94-101, Electronics Complex, Pardeshi Pura,
Indore – 452 010, Madhya Pradesh, India

Unit-2: 90-91, Electronics Complex, Pardeshi Pura,
Indore – 452 010, Madhya Pradesh, India

has established and applies a quality management system for

**Design, Manufacture of Electronic Test & Measuring
Instruments, Training Products for Electrical & Electronics
Education and Providing Technology Training**

An audit was performed, Report No. 07930

Proof has been furnished that the requirements according to

DIN EN ISO 9001: 2000

are fulfilled.

The certificate is valid until 2010-11-20

Certificate Registration No. **85 100 001 07930**



Bangalore, 2007-11-21

The validity of this certificate is subject to timely completion of Surveillance audits as agreed
in the Contract. The Validity of the Certificate can be verified under WWW.tuv.com with the Identification No. 9105027603

The certification Body of
TÜV Rheinland India Pvt. Ltd.

04/11/NABCB/00

www.tuv.com

Low Pass and High Pass Active Filters**AB51****Table of Contents**

1.	Introduction	4
2.	Theory	6
3.	Experiments	
	· Experiment 1	9
	Study of the Active Low Pass Filter	
	· Experiment 2	12
	Study of the Active High Pass Filter	
4.	Data Sheet	15
5.	Warranty	16
6.	List of Accessories	16

RoHS Compliance

Scientech Products are RoHS Complied.

RoHS Directive concerns with the restrictive use of Hazardous substances (Pb, Cd, Cr, Hg, Br compounds) in electric and electronic equipments.

Scientech products are “Lead Free” and “Environment Friendly”.

It is mandatory that service engineers use lead free solder wire and use the soldering irons upto (25 W) that reach a temperature of 450°C at the tip as the melting temperature of the unleaded solder is higher than the leaded solder.

Introduction

AB51 is a compact, ready to use **Active Filters** experiment board. It incorporates Low pass filter and High pass filter on a single board and illustrates the functionality of Active filters at adjustable cutoff frequency. It can be used as stand alone unit with external power supply or can be used with **Scientech Analog lab ST2612** which has built in DC power supply, AC power supply, function generator, modulation generator, continuity tester, toggle switches and potentiometers.

List of Boards :

Model	Name
AB01	Diode characteristics (Si, Zener, LED)
AB02	Transistor characteristics (CB NPN)
AB03	Transistor characteristics (CB PNP)
AB04	Transistor characteristics (CE NPN)
AB05	Transistor characteristics (CE PNP)
AB06	Transistor characteristics (CC NPN)
AB07	Transistor characteristics (CC PNP)
AB08	FET characteristics
AB09	Rectifier Circuits
AB10	Wheatstone Bridge
AB11	Maxwell's Bridge
AB12	De Sauty's Bridge
AB13	Schering Bridge
AB15	Common Emitter Amplifier
AB14	Darlington Pair
AB16	Common Collector Amplifier
AB17	Common Base Amplifier
AB18	Cascode Amplifier
AB19	RC-Coupled Amplifier
AB20	Direct Coupled Amplifier
AB21	Class A Amplifier
AB22	Class B Amplifier (push pull emitter follower)
AB23	Class C Tuned Amplifier
AB25	Phase Locked Loop (FM Demodulator & Frequency Divider / Multiplier)
AB28	Multivibrator (Mono stable / Astable)
AB29	F-V and V-F Converter
AB30	V-I and I-V Converter
AB31	Zener Voltage Regulator
AB32	Transistor Series Voltage Regulator
AB33	Transistor Shunt Voltage Regulator
AB35	DC Ammeter
AB39	Instrumentation Amplifier
AB41	Differential Amplifier (Transistorized)
AB42	Operational Amplifier (Inverting / Non-inverting / Differentiator)

AB51

AB43	Operational Amplifier (Adder/Scalar)
AB44	Operational Amplifier (Integrator/ Differentiator)
AB45	Schmitt Trigger and Comparator
AB49	K Derived Filter
AB52	Active Band Pass Filter
AB54	Tschebyscheff Filter
AB56	Fiber Optic Analog Link
AB57	Owen's Bridge
AB58	Anderson's Bridge
AB59	Maxwell's Inductance Bridge
AB64	RC – Coupled Amplifier with Feedback
AB65	Phase Shift Oscillator
AB66	Wien Bridge Oscillators
AB67	Colpitt Oscillator
AB68	Hartley Oscillator
AB80	RLC Series and RLC Parallel Resonance
AB82	Thevenin's and Maximum power Transfer Theorem
AB83	Reciprocity and Superposition Theorem
AB84	Tellegen's Theorem
AB85	Norton's theorem
AB88	Diode Clipper
AB89	Diode Clampers
AB90	Two port network parameter
AB91	Optical Transducer (Photovoltaic cell)
AB92	Optical Transducer (Photoconductive cell/LDR)
AB93	Optical Transducer (Phototransistor)
AB96	Temperature Transducer (RTD & IC335)
AB97	Temperature Transducer (Thermocouple)
AB101	DSB Modulator and Demodulator
AB102	SSB Modulator and Demodulator
AB106	FM Modulator and Demodulator

..... and many more

Theory

An electric filter is a frequency selective circuit that passes electric signals of specific band of frequencies and attenuates signal of frequencies outside this band. Depending on the type of elements used in their construction filters may be classified as passive or active filters. Elements used in passive filters are resistors, capacitors and inductors. Active filter consists of active components such as Op-amp, transistors with passive elements.

Most commonly used filters are:

1. Low Pass Filter
2. High Pass Filter
3. Band Pass Filter

Low Pass Filter :

It is a frequency selective circuit, which passes signals of frequency below it's high cut off frequency (f_h) and attenuates signals of frequency above f_h .

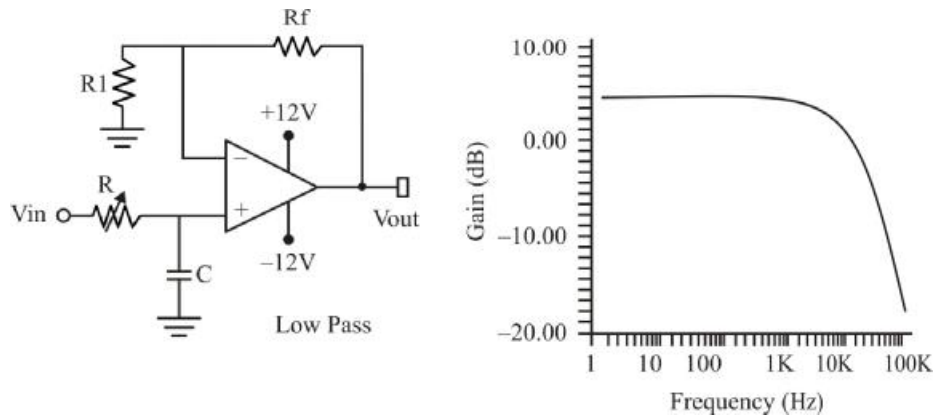


Figure 1

Equation of low pass filter is

$$\frac{V_{out}}{V_{in}} = \frac{AE}{1 + j(f/f_h)}$$

—————→ 1

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{A_f}{\{1 + (f/f_h)^2\}^{1/2}}$$

—————→ 2

V_{in} = Input signal Voltage

V_{out} = Output signal Voltage

$$\left| \frac{V_{out}}{V_{in}} \right| = \text{Gain of filter as a function of frequency}$$

$$AF = 1 + R_F / R_1 = \text{pass band gain of filter}$$

f = frequency of input signal

$f_H = 1/2\pi RC$ = high cut off frequency, 3-db frequency, corner frequency
 Operation of low pass filter using equation 2

- a. at low frequencies $f < f_c$ $\left| \frac{V_{out}}{V_{in}} \right| = A_f$
- b. at $f = f_c$ $\left| \frac{V_{out}}{V_{in}} \right| = 0.707 * A_f$
- c. at $f > f_c$ $\left| \frac{V_{out}}{V_{in}} \right| < A_f$

The ideal low pass filter has a constant gain A_f from 0 to high cut off frequency (f_H) at f_H the gain is $0.707 * A_f$. And after f_H it decreases at a constant rate with an increase in frequency i.e. when input frequency is increased tenfold (one decade), the voltage gain is divided by 10.

$$\text{Gain (db)} = 20 \log |V_{out} / V_{in}|$$

i.e. Gain Roll off rate is $-20\text{db} / \text{decade}$.

High Pass Filter :

It is a frequency selective circuit, which passes signals of frequencies above it's low cut off frequency (f_L) and attenuates signals of frequencies below f_L .

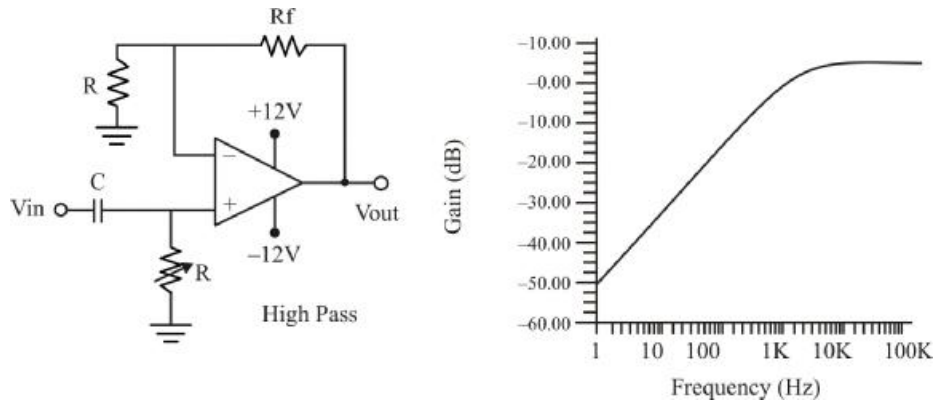


Figure 2

Equation of High pass filter is

$$\frac{V_{out}}{V_{in}} = \frac{A_f}{1 + j(f/f_c)} \quad \longrightarrow \quad 3$$

$$\frac{V_{out}}{V_{in}} = \frac{A_f}{\{1 - (f/f_c)^2\}^{1/2}} \quad \longrightarrow \quad 4$$

V_{in} = Input signal Voltage

V_{out} = Output signal Voltage

$$\left| \frac{V_{out}}{V_{in}} \right| = \text{Gain of filter as a function of frequency}$$

$A_F = 1 + R_F / R_1$ = pass band gain of filter

f = frequency of input signal

$f_L = 1/2 \pi RC$ = Low cut off frequency, 3-db frequency, corner frequency
Operation of high pass filter using equation.

a. at low frequencies $f < f_L$ $\left| \frac{V_{out}}{V_{in}} \right| < A_F$

b. at $f = f_L$ $\left| \frac{V_{out}}{V_{in}} \right| = 0.707 * A_{F(\text{pass})}$

c. at $f > f_L$ $\left| \frac{V_{out}}{V_{in}} \right| < A_F$

In ideal high pass filter, when $f < f_L$ gain is increased at a constant rate has a constant rate with an increase in frequency. At f_L the gain is $0.707 * A_F$. And above f_L it has constant gain of A_F . Below f_L when input frequency is increased tenfold (one decade), the voltage gain is multiplied by 10.

$$\text{Gain (db)} = 20 \log | V_{out} / V_{in} |$$

i.e. Gain Roll off rate is $-20\text{db} / \text{decade}$.

Experiment 1

Objective :

Study of the Active Low Pass Filter and to Evaluate :

- High cutoff frequency of Low pass filter.
- Pass band gain of Low Pass Filter.
- Plot the frequency response of Low Pass Filter.

Equipments Needed :

1. Analog board of **AB51**.
2. DC power supplies +12V, -12V from external source or **ST2612 Analog Lab**.
3. Function generator or **ST2612 Analog Lab**.
4. Oscilloscope
5. Digital Multimeter
6. 2 mm patch cords.

Circuit diagram :

Circuit used to study Active Low pass filter shown in figure 3.

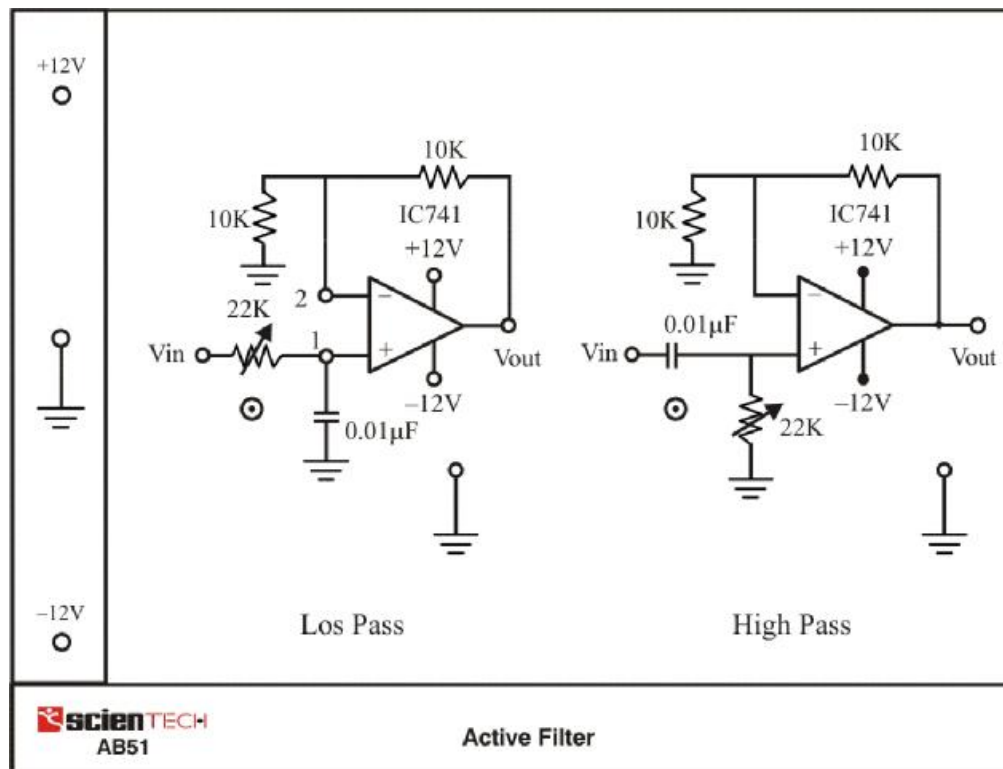


Figure 3

Procedure :

1. Connect Ohmmeter between Test point Vin and Test point 1. Adjust resistance value to 1.59K by varying the potentiometer 22K of Low pass filter to set the high cutoff frequency (f_H) at 10K.
2. Connect +12V and -12V DC power supplies at their indicated position from external source or **ST2612 Analog Lab**.
3. Switch 'On' the power supply.
4. Connect a sinusoidal signal of amplitude 1V (p-p) of frequency 1KHz to Vin of Low Pass Filter from external source or **ST2612 Analog Lab**.
5. Observe output on oscilloscope by connecting Test point Vout to oscilloscope.
6. Increase the frequency of input signal step by step and observe the effect on output Vout on oscilloscope.
7. Tabulate values of Vout, gain, gain (db) at different values of input frequency shown in observation Table.

Observation Table :

Sr. No.	Input frequency (Hz)	Vout	$ V_{out} / V_{in} = \text{gain}$	Gain(db) = $20 \text{ Log } V_{out} / V_{in} $
1	500			
2	1 K			
3	5 K			
4	10 K (f_H)			
5	15 K			
6	20 K			
7	30 K			

8. Plot the frequency response of low pass filter using the data obtained at different input frequencies.

9. Perform the same procedure at different Cutoff frequencies as shown below:

Resistance (W)	Capacitance (uF)	f_H high cutoff frequency (Hz)
800	0.01	20K
1.59 K	0.01	10K
15.9 K	0.01	1K

Theoretical Calculations :

Calculate all the following values

1. Pass band gain of Low pass filter $A_F = 1 + R_F / R_1$
2. Pass band gain (db) = $20 \log |V_{out} / V_{in}|$
3. 3 db frequency $f_H = 1/2\pi RC$
4. Gain at 3 db frequency $f_H = 0.707 * A_F$
5. Gain (db) at 3 db frequency $f_H = 20 \log |V_{out} / V_{in}|$ where $V_{out} = (2)^{1/2} * V_{in}$
6. Roll off rate = -20db/decade

Results :

	Theoretical	Practical
Pass band gain(A_f)		
Pass band gain(A_f) in db		
3db frequency f_H		
Gain at 3db frequency (f_H) in db		

Experiment 2

Objective :

Study of the Active High Pass Filter and to Evaluate :

1. Low cutoff frequency of Low pass filter.
2. Pass band gain of High pass filter.
3. Plot the frequency response of High pass filter.

Equipments Needed :

1. Analog board of AB51.
2. DC power supplies +12V, -12V from external source or ST2612 Analog Lab.
3. Function generator or ST2612 Analog Lab.
4. Oscilloscope
5. Digital Multimeter
6. 2 mm patch cords.

Circuit Diagram :

Circuit used to study Active High pass filter shown in figure 4.

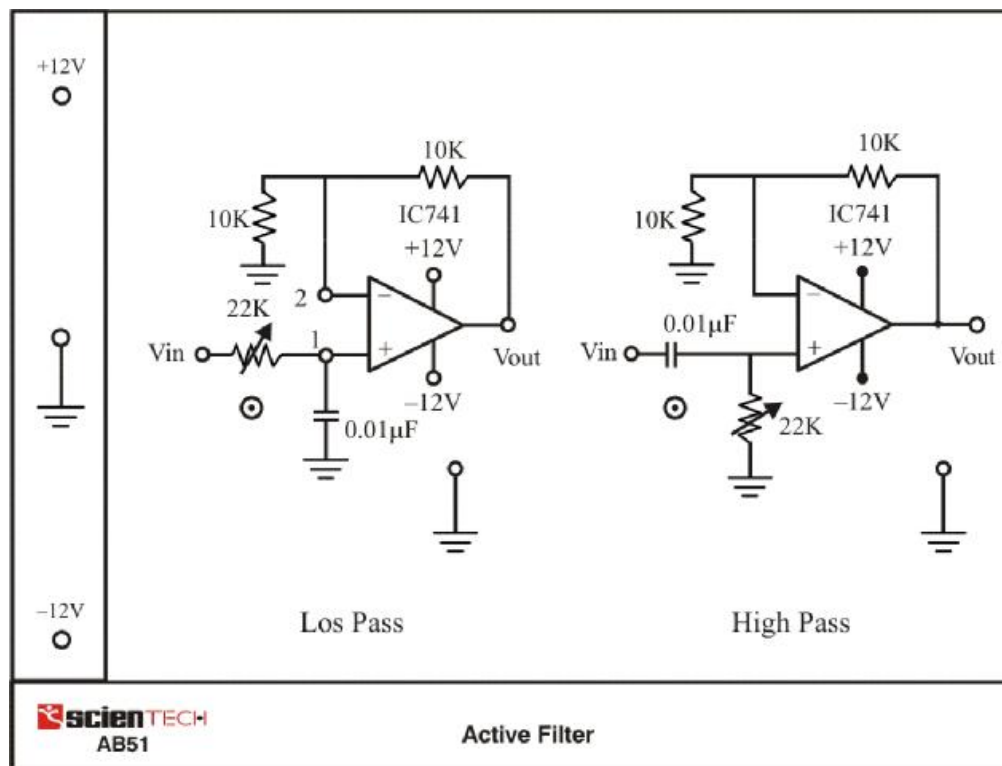


Figure 4

Procedure :

1. Connect Ohmmeter between V_{in} and Test point 3. Adjust resistance value to 15.9K by varying the potentiometer 22K of High pass filter to set the Low cutoff frequency (f_L) at 1K.
2. Connect +12V and -12V DC power supplies at their indicated position from external source or **ST2612 Analog Lab**.
3. Switch 'On' the power supply.
4. Connect a sinusoidal signal of amplitude 1V (p-p) of frequency 100 Hz to the Test point V_{in} of high pass filter from external source or **ST2612 Analog Lab**.
5. Observe output on oscilloscope by connecting Test point V_{out} to oscilloscope.
6. Increase the frequency of input signal step by step and observe the effect on output V_{out} on oscilloscope.
7. Tabulate different values of V_{out} , gain, gain (db) at different values of input frequency shown in observation Table.

Observation Table :

Sr. No.	Input frequency (Hz)	V_{out}	$ V_{out} / V_{in} = \text{gain}$	Gain(db) = $20 \text{ Log } V_{out} / V_{in} $
1	100			
2	200			
3	500			
4	1K(f_L)			
5	5 K			
6	10 K			
7	15 K			
8	20 K			

AB51

8. Plot the frequency response of high pass filter using the data obtained at different input frequencies.
9. Perform the same procedure at different Cutoff frequencies as shown below:

Resistance (W)	Capacitance (μ F)	3 db frequency (Hz)
800	0.01	20K
1.59 K	0.01	10K
15.9 K	0.01	1K

Theoretical Calculations :

Calculate all the following values

1. Pass band gain of Low pass filter $A_F = 1 + R_F / R_I$
2. Pass band gain (db) = $20 \log |V_{out} / V_{in}|$
3. Low cutoff frequency $f_L = 1/2\pi RC$
4. Gain at Low cutoff frequency $f_L = 0.707 * A_F$
5. Gain (db) at Low cutoff frequency $f_H = 20 \log |V_{out} / V_{in}|$ where
 $V_{out} = (2)^{1/2} * V_{in}$
6. Roll off rate = -20db/decade

Results :

	Theoretical	Practical
Pass band gain(A_f)		
Pass band gain(A_f) in db		
Low cutoff frequency (f_L)		
Gain at 3db frequency (f_L) in db		



UA741

GENERAL PURPOSE
SINGLE OPERATIONAL AMPLIFIER

- LARGE INPUT VOLTAGE RANGE
- NO LATCH-UP
- HIGH GAIN
- SHORT-CIRCUIT PROTECTION
- NO FREQUENCY COMPENSATION
- REQUIRED
- SAME PIN CONFIGURATION AS THE UA709


DESCRIPTION

The UA741 is a high performance monolithic operational amplifier constructed on a single silicon chip. It is intended for a wide range of analog applications.

- Summing amplifier
- Voltage follower
- Integrator
- Active filter
- Function generator


The high gain and wide range of operating voltages provide superior performances in integrator, summing amplifier and general feedback applications. The internal compensation network (6dB/octave) insures stability in closed loop circuits.

PIN CONNECTIONS (top view)

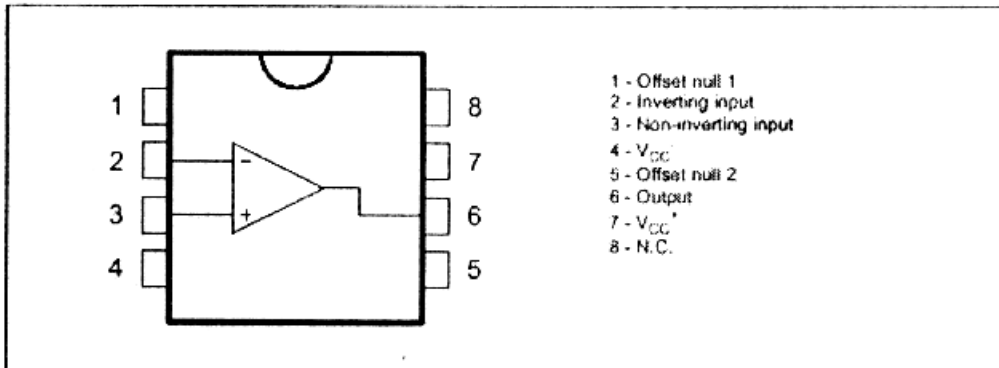

November 2001

1/5

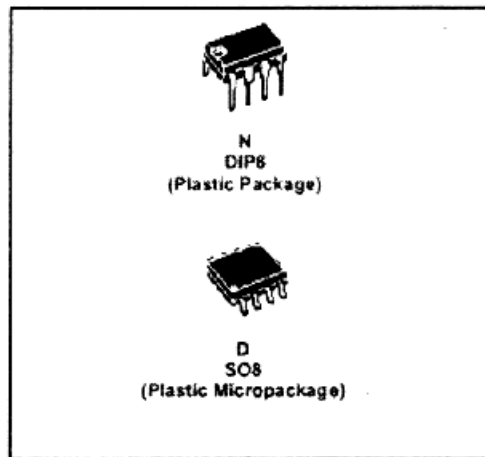

ORDER CODE

Part Number	Temperature Range	Package	
		N	D
UA741C	0°C, +70°C	•	•
UA741I	-40°C, +105°C	•	•
UA741M	-55°C, +125°C	•	•

Example : UA741CN

N = Dual in Line Package (DIP)
D = Small Outline Package (SO) - also available in Tape & Reel (TR)

Warranty

1. We guarantee the product against all manufacturing defects for 24 months from the date of sale by us or through our dealers. Consumables like dry cell etc. are not covered under warranty.
2. The guarantee will become void, if
 - a) The product is not operated as per the instruction given in the operating manual.
 - b) The agreed payment terms and other conditions of sale are not followed.
 - c) The customer resells the instrument to another party.
 - d) Any attempt is made to service and modify the instrument.
3. The non-working of the product is to be communicated to us immediately giving full details of the complaints and defects noticed specifically mentioning the type, serial number of the product and date of purchase etc.
4. The repair work will be carried out, provided the product is dispatched securely packed and insured. The transportation charges shall be borne by the customer.

For any Technical Problem Please Contact us at service@scientech.bz

List of Accessories

1. 2mm Patch Cord (Red) 16" 2 Nos.
2. 2mm Patch Cord (Black) 16" 2 Nos.
3. 2mm Patch Cord (Blue) 16" 3 Nos.
4. e-Manual 1 No.

Updated 26-06-2009